# POST GRADUATE COMMON ENTRANCE TEST - 2011

DATE and TIME		COURSE	SUBJECT
06-08-2011 10:30 am to 12:30 pm	ME / M. Tech / MBA (Infrastructure Management ) courses offered by VTU / UVCE / UBDTCE		
MAXIMUM MARKS		TOTAL DURATION	MAXIMUM TIME FOR ANSWERING
		150 Minutes	120 Minutes
MENTION YOUR PGCI	ET NO.	QUESTION	BOOKLET DETAILS
TOP BEAL ST		VERSION CODE	SERIAL NUMBER
oT mov		$\mathbf{A}_3$	00006435

#### DOs

- 1. Check whether the PGCET No. has been entered and shaded in the respective circles on the OMR answer sheet.
- 2. This question booklet is issued to you by the invigilator after the 2nd Bell, i.e. after 10:25 am.
- 3. The serial number of this question booklet should be entered on the OMR answer sheet.
- 4. The version code of this question booklet should be entered on the OMR answer sheet and the respective circles should also be shaded completely.
- 5. Compulsorily sign at the bottom portion of the OMR answer sheet in the space provided

#### DON'Ts

- 1. The timing and marks printed on the OMR answer sheet should not be damaged / mutilated / spoiled.
- The 3rd Bell rings at 10:30 am, till then;
  - Do not remove the seals of this question booklet.
  - Do not look inside this question booklet.
  - Do not start marking on the OMR answer sheet.

#### IMPORTANT INSTRUCTIONS TO CANDIDATES

- This question booklet contains 75 (items) questions and each question will have one statement and four answers. (Four different options / responses.)
- After the 3rd bell is rung at 10:30 am, remove the seals of this question booklet and check that this booklet does not
  have any unprinted or torn or missing pages or items etc., if so, get it replaced by a complete test booklet. Read
  each item and start marking on the OMR answer sheet.
  - During the subsequent 120 minutes :
     Read each question (item) carefully.
    - Choose one correct answer from out of the four available responses (options / choices) given under each question / item. In case you feel that there is more than one correct response, mark the response which you consider the best. In any case, choose only one response for each question / item.
    - Completely darken / shade the relevant circle with a blue or black ink ballpoint pen against the question number on the OMR answer sheet.
- Please note that even a minute unintended ink dot on the OMR answer sheet will also be recognized and recorded by the scanner. Therefore, avoid multiple markings of any kind on the OMR answer sheet.
- Use the space provided at the bottom on each page of the question booklet for Rough Work. Do not use the OMR answer sheet for the same.
- After the last bell is rung at 12:30 pm, stop marking on the OMR answer sheet and affix your left hand thumb impression on the OMR answer sheet as per the instructions.
- Hand over the OMR answer sheet to the room invigilator as it is.
- 8. After separating the top sheet (KEA copy), the invigilator will return the bottom sheet replica (candidate's copy) to you to carry home for self evaluation.
- Preserve the replica of the OMR answer sheet for a minimum period of ONE year.
- Only Non-programmable calculators are allowed.
- 11. Please note this Question Booklet consists of *sub*-branches. Total number of questions is 75. Question Nos. 1 to 45 is compulsory and common to all the branches. Candidate has to answer *any one* paper from Question Nos. 46 75 out of the *sub*-branches as opted, by him/her in the Application Form.

## **Marks Distribution**

PART – A: (Section-I) 30 Questions:  $30 \times 1 = 30$ ; (Section-II): 15 Questions:  $15 \times 2 = 30$ PART – B: (Section-I) 20 Questions:  $20 \times 1 = 20$ ; (Section-II): 10 Questions:  $10 \times 2 = 20$  Electrical Sciences

# ELECTRICAL SCIENCES

#### IMPORTANT INSTRUCTIONS AND BRANCHWISE INDEX FOR THE CANDIDATES

Question Nos. 1 to 45 is compulsory and common to all the branches. Question Nos. 46 to 75 are optional. Sub-branches are there in this Booklet. The candidate has to opt any one branch according to his/her Application Form.

язил	VERSION CODE SERIAL NU		Page	Page No.		
Sub- branch	GSF30000 Subject			То		
1.	Electrical and Ele	ectronics Engineering (E & E)	17	22		
2.	Electronics and 6	23	28			
belion	Telecommunicati	on Engineering (TC)	an ban onin'i			
3.	Bio-Medical Engi & Medical Electron	Telephone in treating and in season on a season of the sea	29	34		
4.	Instrumentation	maco de earch older em subagaro, anila w nortago doss bas enedeado (anila) é Campleod (al	35	39		

## PART - A

# ( Common to E&E/E&C/TC/BME/ME/IT ) SECTION – I

Each question carries one mark.

 $30 \times 1 = 30$ 

1.  $\int (2\cos x - 4\sin x) \, dx \text{ is}$ 


(A)  $2\sin x + 4\cos x$ 

(B)  $2\sin x - 4\cos x$ 

(C)  $2\sin x - 4\cos x + c$ 

(D)  $2\sin x + 4\cos x + c$ .

2.

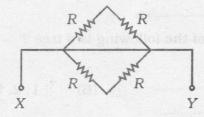

The resistance between x-y terminals is


(A) R

(B)  $\frac{R}{2}$ 

(C) zero

(D)  $\frac{R}{4}$ .

3.

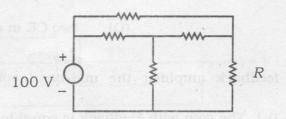

In the figure, the power dissipated by the resistor R is 10 W. If the voltage is increased to 110 V, the power dissipated will be

(A) 12·1 W

(B) 21 W


(C) 20 W

(D) depends on value of R.

- 4. In a series RLC circuit, we get a leading power factor current
  - (A) at resonant frequency

- (B) at less than resonant frequency
- (C) at greater than resonant frequency (D)
  - o) at all frequencies.

5.

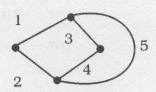

In the graph shown which of the following is a tree?

 $(A) \{1, 2, 3\}$ 

(B)  $\{1, 2, 5\}$ 

(C) {3, 4, 5}

- (D)  $\{1, 2, 3, 4\}.$
- 6. In a transistor configuration, the voltage gain is found to be 1. The configuration is
  - (A) CE

(B) CB

(C) CC


- (D) Two CE in cascade.
- 7. In a voltage-series feedback amplifier the mid-band voltage gain is 1200. The feedback factor  $\beta$  = 0·1. The gain with feedback is equal to
  - (A) 1200

(B) -120


(C) -991.7


(D) -9.917.

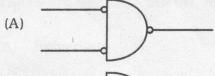- 8. The distortion introduced by the non-linear dynamic transfer characteristics may be reduced using
  - (A) push-pull amplifier configuration
  - (B) positive feedback amplifier
  - (C) cascading amplifier
  - (D) increasing source impedance.
- 9. Which of the following represents a NAND gate?



(B)

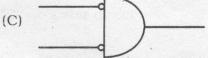

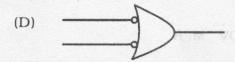


- 10. The BCD code for decimal number 12 is
  - (A) 00001100

(B) 10000010

(C) 00010010

(D) 11000000.

11.

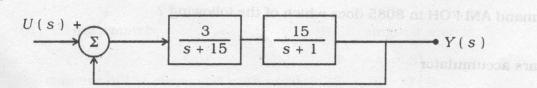

The steady state error in the response of the above system to a unit step input is

(A) 25%

101 (B) (B) 0.75% 10 1000 and 10 1000

(C) 6%

(D) 33%

12. A code segment of 8085 is given l	12.	below	
---------------------------------------	-----	-------	--

LXI H, 3FFE

MOV B, M

INR L

MOV A. M

ADD B

INR L

MOV M, A

On completion of execution, the result of addition is found in

(A) register A

(B) location 2FFE

(C) location 2F00

- (D) location 3000.
- 13. The command ANI FOH in 8085 does which of the following?
  - (A) Clears accumulator
  - (B) Clears the lower nibble of the accumulator
  - (C) Clears the upper nibble of the accumulator
  - (D) Sets the lower nibble of the accumulator.

14. The contents of the accumulator in 8085 is A7 and CY = 0. After the execution of the instruction RLC, the contents of accumulator and CY are

(8)

- (A) [A] = A8; CY = 0
- [A] = 4E; CY = 1(B)
- [A] = 4F; CY = 0
- (D) [A] = A8; CY = 1.
- The instruction STA 2080H, in 8085 is of which addressing mode? 15.
  - Immediate (A)
  - Register direct (B)
  - Direct (C)
  - (D) Register indirect.
- 21. A voltage source is connected across an ideal inductor The current through  $\begin{bmatrix} 2 & 1 & 1 \\ 2 & 0 \end{bmatrix}$ 0 is a/an 16.
  - symmetric matrix (A)

skew-symmetric matrix (B)

7 is

0

20. The solution of the equation  $x + y \frac{dy}{dt} = 0$  is

identity matrix (C)

(D) singular matrix.

8

- 3(s+10), in the frequency domain. The value The current in a cheam 6 44-by 8 The cofactor of the element 8 in the matrix 2 5 9
  - (A) 9

9 (B)

(C) 33

-33.(D)

- 18. The angle  $\theta$  between two vectors  $\vec{a}$  and  $\vec{b}$  is given by
  - (A)  $\cos \theta = \frac{|\vec{a} \times \vec{b}|}{|\vec{a} \cdot \vec{b}|}$

(B)  $\cos \theta = \frac{|\overrightarrow{a} \times \overrightarrow{b}|}{|\overrightarrow{a}| |\overrightarrow{b}|}$ 

(C)  $\tan \theta = \frac{|\vec{a} \times \vec{b}|}{|\vec{a}||\vec{b}|}$ 

- (D)  $\sin \theta = \frac{|\vec{a} \times \vec{b}|}{|\vec{a}||\vec{b}|}$
- 19. The magnitude of the position vector of the point (2, 3, -4) is
  - (A)  $\sqrt{11}$

(B) C

(C) √29

- (D) 1.
- 20. The solution of the equation  $x + y \frac{dy}{dx} = 0$  is
  - $(A) \quad x + y = k$

 $(B) \qquad x^2 + y^2 = k$ 

(C)  $\sqrt{x} + \sqrt{y} = k$ 

- (D) ln(x+y)=k.
- 21. A voltage source is connected across an ideal inductor. The current through th inductor is observed to be a constant. The voltage source must be
  - (A) sinusoidal

(B) ramp

(C) step

- (D) impulse.
- 22. The current in a circuit is given by  $I(s) = \frac{3(s+10)}{s(s+12)}$ , in the frequency domain. The value

of i(t) as  $t \to \infty$  is

(A) 0.5 A

(B) 0 A

(C) 3 A

(D) 2·5 A.

23. The relationship between the electric field intensity and the potential is given by

(A)  $E = -\nabla V$ 

(B)  $E = \int V \cdot dl$ 

(C)  $E = \nabla^2 V$ 

(D)  $E = \nabla \times V$ .

24. A full-wave rectifier circuit is supplied by a centre-tap transformer. The peak voltage from end terminal to centre tap is 135 V. Neglecting the forward resistance of the diode, the d.c. output voltage is

(A) 135 V

(B) 95·45 V

(C) 85.94 V

(D) 270 V.

25. In a fixed bias circuit,  $V_{CC}$  = 12 V and  $R_b$  = 1 M $\Omega$ . If an n-p-n silicon transistor is used, the base current  $I_B$  is equal to


(A) 12 μA

(B) 11·4 μA

(C) 12 A

(D) 3·46 μA.

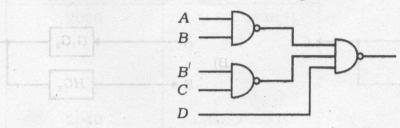26. The output of the network shown below is given by



(A)  $AB + B^{\prime}C + D$ 

(B)  $AB + B^{\prime}C + D^{\prime}$ 

(C) (A+B)(B'+C)(D)

(D) (A+B)(B'+C)(D').

27. A counter is designed with T flip-flops. The present state is '011' and the next state is '010'. The input to the T flip-flop to have correct state transition at the next clock pulse is


(A) 001

(B) 011

(C) 010

(D) 111.

28.

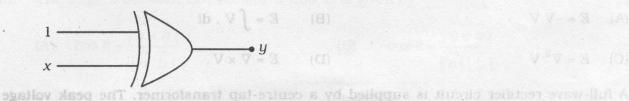

In the above gate the relation between x and y is


(A) y = x

(B) y = 1 batter include a batter abold


(C) y = x


(D) y = 0.

29.

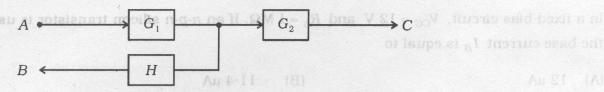

The equivalent for the block diagram is

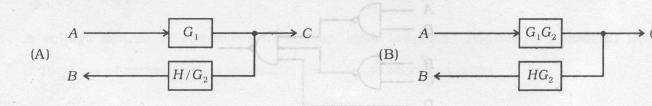

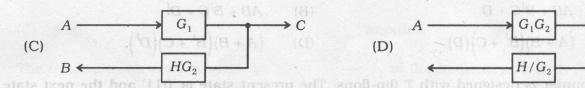

- 30. The characteristic equation of a system is given by  $2s^4 + s^3 + 3s^2 + 5s + 7 = 0$ . The number of roots that lie in the right half of s plane is
  - (A) zero

(B) 2

(C) 4


(D) 1.

#### SECTION - II

Each question carries two marks.

 $15 \times 2 = 30$ 

31.

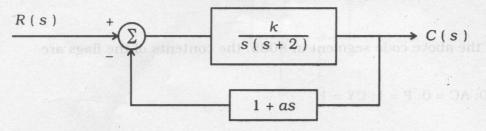

In the above figure damping ratio  $\xi = 0.7$  and undamped natural frequency  $\omega_n = 4 \text{ rad/sec}$ . The values of k and a are

(A) 
$$k = 16$$
,  $a = 0.225$ 

(B) 
$$k = 8, a = 0.225$$

(C) 
$$k = 16, a = 0.455$$

(D) 
$$k = 64, a = 0.9$$
.

32.

C

C

Address	Instruction
2000	LXI SP, 2800 H
	I I I I I I I I I I I I I I I I I I I
2040	CALL 2060 H
• • • • •	1 9 9
• 10	
•	.03

In the above segment of 8085, what are the contents of the stack and stack pointer after CALL instruction is executed?

(A) 2040, 2800

(B) 2041, 2401

- (C) 2060, 2800
- (D) 2043, 27FE.

33. MVI B, 96H

MVI A, 97H

ADD B

On execution of the above code segment in 8085, the contents of the flags are

(A) 
$$S = 0$$
;  $Z = 0$ ;  $AC = 0$ ;  $P = 1$ ;  $CY = 1$ 

(B) 
$$S = 1$$
;  $Z = 1$ ;  $AC = 0$ ;  $P = 0$ ;  $CY = 1$ 

(C) 
$$S = 0$$
;  $Z = 0$ ;  $AC = 0$ ;  $P = 0$ ;  $CY = 1$ 

(D) 
$$S = 0$$
;  $Z = 1$ ;  $AC = 0$ ;  $P = 1$ ;  $CY = 1$ .

34. The characteristic table of an X-Y flip-flop is given below to be implemented using J-K flip-flop. The J-K inputs are

X	Y	$g_{n+1}$
0	0	1
0	1	$Q_n$
1	0	$\overline{Q}_n$
air pirco	344 jus 16	0.80


(A) J = X;  $K = \overline{Y}$ 

(B)  $J = \overline{X}; K = Y$ 

(C) J = Y;  $K = \overline{X}$ 

(D)  $J = \overline{Y}; K = X.$ 

35.

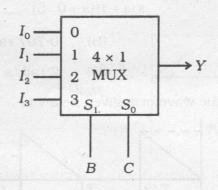

The Boolean function F ( A, B, C ) =  $\Sigma$  ( 1, 3, 5, 6 ) is to be implemented with a  $4 \times 1$  MUX as shown. The inputs  $I_0$ ,  $I_1$ ,  $I_2$ ,  $I_3$  are


(A) 01AA'

(B)  $10 A A^{\prime}$ 

(C) 00 A' A

(D) 11 A' A.

36.

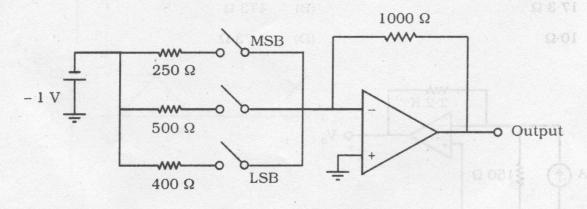

For switch position 1 1 0 (1 is close and 0 is open ) the output voltage is

(A) 2 V

(B) 4 V

(C) 6 V

(D) 0 V.

37. For the transfer function  $G(s)H(s) = \frac{1}{s(s+1)(s+0.5)}$  the phase cross-over frequency is


(A) 0.5 rad/s

(B) 0.707 rad/s

(C) 1.732 rad/s

(D) 2 rad/s.

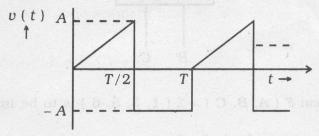38. The rms value of the periodic waveform given below is



(A)  $\sqrt{\frac{2}{3}}A$ 

(B)  $\sqrt{\frac{3}{2}}A$ 

(C)  $\sqrt{\frac{1}{3}} A$ 

(D)  $\sqrt{2} A$ 

39. The line current drawn by a balanced star connected resistive load from a 173 V 3-6 supply is 10 A. The load resistance per phase is


(A) 17·3 Ω

(B) 173 Ω

(C) 10 Ω

(D)  $1.73 \Omega$ .

40.

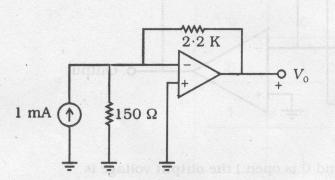

In the circuit  $v_0$  is equal to

(A) 2·2 V

(B) -2.2 V

(C) 1.5 V

(D) -1.5 V.

16 V

4 V

 $t_1'$ 

 $t_1$ 

(D)

42. What value of x in the given matrix will make it singular?

[8]	x	0]
4	0	0 2 0
8 4 12	6	0


- (A) 4
- (C) 8

- (B) 6

12.

(D)

43.

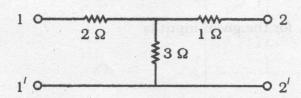


The [Y] parameters of the two port network are given by

- $(A) \quad \begin{bmatrix} 5 & 3 \\ 3 & 4 \end{bmatrix}$
- (C)  $\begin{bmatrix} 2 & 3 \\ 3 & 1 \end{bmatrix}$

- (B)  $\begin{bmatrix} 0.833 & 0.5 \\ 0.5 & 0.667 \end{bmatrix}$
- (D)  $\begin{bmatrix} 0.3636 & -0.2727 \\ -0.2727 & 0.4545 \end{bmatrix}$

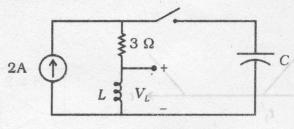44. In the circuit shown, steady state is reached with switch open. The switch is closed at t = 0. At  $t = 0^+$ , the voltage  $V_L$  is,



(A) 0 V

(B) 6 V

(C) - 6V

(D) 2 V.

45. A system function is given by  $\frac{V(s)}{I(s)} = \frac{1}{s+3}$ . If i(t) = u(t) (unit step), v(t) is

(A)  $e^{-3i}$ 

(B)  $1 - e^{-3t}$ 

(C)  $1 - 3e^{-3t}$ 

(D)  $\frac{1}{3} - \frac{1}{3}e^{-3t}$ .

Note:

Please choose to answer part - B below corresponding to your basic degree.

has afglow at high ad hittoric if

#### PART - B

# (E & E: ELECTRICAL AND ELECTRONICS ENGINEERING)

#### SECTION - 1

Each question carries one mark.

 $20 \times 1 = 20$ 

- 46. An alternator running at 3000 rpm generates voltage of 50 Hz. The number of poles of the alternator will be said a said and the s

(A) 8 poles and of the poles (B) 6 poles

(C) 4 poles

at

- (D) 2 poles.
- 47. Run-away speed of a pelton wheel is
  - full-load speed (A)
  - (B) actual speed operating at no-load
  - no-load speed when governor mechanism fails (C)
  - (D) 80% greater than the normal speed.
- 48. The input-output equation of a 0.5 MW powerhouse is given by  $I = 30 + 0.8L + 0.5L^2$ , where I is in millions of keal per hour and L is in megawatts.

The input when the plant is running at no-load will be

0.5 kcal/hr (A)

(B) 21.3 kcal/hr

(C)  $30 \times 10^6$  kcal/hr

30 kcal/hr.

- 49. The conductors used for transmitting power must have which of the followin
  - (A) It should have low value of specific resistance
  - (B) It should be light in weight and non-brittle
  - (C) It should have low cost and high tensile strength
  - (D) All of these.
- 50. Ferranti effect on long overhead lines is experienced when
  - (A) the line is lightly loaded
- (B) the power factor is unity
- (C) the power factor is loading
- (D) corona effect is dominant.
- 51. The percentage reactance can be converted into ohmic value with which of the following formulae?

(A) 
$$X_{\text{ohms}} = \frac{X(\%) \times 100 (\text{kV})^2}{\text{kVA}}$$


(B) 
$$X_{\text{ohms}} = \frac{X(\%) \times 1000 (\text{kV})^2}{\text{kVA}}$$

(C) 
$$X_{\text{ohms}} = \frac{X(\%) \times (\text{kV})^2}{1000 \text{ (kVA)}}$$

(D) 
$$X_{\text{ohms}} = \frac{X(\%) \times (10) \times (kV)^2}{kVA}$$
.

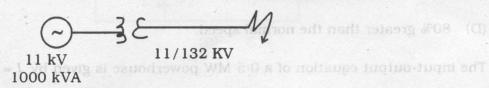52. For the system shown below the base voltage is,

elial malasibem Transmission line as beel on Ol



- (A) 11 kV for the system
- (B) 132 kV for the system
- (C) 11 kV for generator and 132 kV for transmission line
- (D) cannot be determined for the given data.

ne

59.	The	no-load current of a transformer in t	terms o	f full-load current is usually
	(A)	1% to 3%	(B)	3% to 15%
	(C)	9% to 12%	(D)	12% to 20%.
60.	The	concentric windings are used in core	e-type t	ransformers with
	(A)	HT winding placed next to core	(B)	LT winding placed next to core
	(C)	LT winding on the outer side	(D)	None of these.
61.	The	skin effect increases the effective val	ue of	turnique entertiel off to don't be
	(A)	resistance of the conductor		more
	(B)	reactance of the conductor		
	(C)	capacitance of the conductor		The second secon
	(D)	inductance & capacitance of the cor	iductor	
62.	The	major advantage of a bridge rectifier	is that	
	(A)	no centre-tap transformer is require	d	
	(B)	the required peak inverse voltage of rectifier	of each	diode is double of that for a full-wave
	(C)	peak inverse voltage of each diode is	s half o	f that for a full-wave rectifier
	(D)	the input is more smooth.		
63.	In a	thyristor, holding current is		
	(A)	more than latching current	(B)	less than latching current
	(C)	equal to latching current	(D)	zero. No objeto nelestromo ostro. Ve
64.	The	function of snubber circuit connected	d acros	s an SCR is to
	(A)	suppress dv/dt	(B)	increase $dv/dt$
	(C)	decrease dv/dt	(D)	none of these.
65.		a 3-phase, six-pulse diode rectification $V_m$ is		

(A)  $\frac{3\sqrt{2}}{\pi} V_m$  (B)  $\frac{3V_m}{\pi}$  (C)  $\frac{3\sqrt{3}}{2\pi} V_m$  (D)  $\frac{3\sqrt{3}}{\pi} V_m$ .

#### SECTION - II

Each question carries two marks.

 $10 \times 2 = 20$ 

- 66. A transformer has a core loss of 64 W and copper loss of 144 W, when it is carrying 20% overload current. The load at which this transformer will operate at the maximum efficiency is
  - (A) 80%

(B) 66%

(C) 120%

- (D) 44%.
- 67. In a 3-phase star connected alternator a field current of 40 A produces full-load current of 200 A on short circuit and 1160 V an open circuit. If the resistance of the alternator is  $0.5~\Omega$ , then the value of synchronous reactance is
  - (A) 5.78 Ω

(B)  $16.5 \Omega$ 

(C) 3·31 Ω

- (D) 29 Ω.
- 68. The forward breakover voltage of a thyristor is 175 volts with a gate pulse of 2 mA. The conduction angle for a sinusoidal voltage of 350 V ( peak ) is
  - (A) 0°

(B) 30°

(C) 60°

- (D) 90°.
- 69. An SCR can be triggered with a  $\frac{dv}{dt}$  of 200 V/ $\mu$ s. If the charging current flowing through the junction is 5 mA, the equivalent capacitance of depletion layer is
  - (A) 20 pF

(B) 25 F

(C) 25 pF

- (D) 250 pF.
- 70. A 4-pole lap wound armature has 480 conductors and a flux per pole of 25 mWb. The *emf* generated when running at 600 rpm, will be
  - (A) 240 V

(B) 120 V

(C) 60 V

(D) 30 V.

71. Three units of 1:5 transformers are connected in  $\Delta$  – Y to supply a 3-phase load from

	u 1.	oo v, 3-pnase sour	ce. The line v	ortuge on the		
	(A)	1000 V		(B)		20% avertoad curr
	(C)	3464 V		(D)	803 V.	efficient yes contin
72.	A tr	ansmission line is	transmitting	a fixed am	ount of power w	hose efficiency increase
	whe	en				
	(A)	voltage decreases	and power fa	ctor remai	ns constant	
	(B)	voltage increases	and power fa		creases	
	(C)	voltage decreases	and power fa			
	(D)	voltage is constan	t and power	factor decre	eases.	
79		the residented pools	29.92			Q 18.8 (2)
73.		cates 100 amp and		at misery in		in which the ammeter
	(A)	0.95		(B)	0.78	
	(C)	0.65		(D)	0.55.	
74.				acting SCR	is 10A. If its ga	te current is made hal
	tne	anode current will	become			through the june're
	(A)	0 A		(B)	5 A	
	(C)	10 A		(D)	20 A.	
75.	The	p.u. impedance val	lue of an alte	rnator corr	esponding to bas	se values of 13·2 kV an
	30 N	MVA is 0.2 p.u. The	p.u. value fo	r the base	values of 13.8 kV	and 50 MVA will be
	(A)	0·106 p.u.		(B)	0·206 p.u.	(A) 240 V
`	(C)	0·306 p.u.		(D)	0·318 p.u.	
			TREW!	OR ROUGH	SPACE	

m

es

er

f,

d

#### PART - B

# (E & C and TC : ELECTRONICS & COMMUNICATION ENGINEERING & TELECOMMUNICATION ENGINEERING)

#### SECTION - I

Each question carries one mark.

 $20 \times 1 = 20$ 

- 46. For fast switching applications, a power diode should have
  - (A) low on state voltage and low breakdown voltage
  - (B) high on state voltage and high breakdown voltage
  - (C) large reverse recovery time
  - (D) small reverse recovery time.
- 47. In a single-phase full-wave A.C. voltage controller with R & L load, if  $\beta = 205^{\circ}$  and delay angle  $\alpha = \pi/4$ , then the conduction angle of a thyristor is
  - (A) 280°

(B) 220°

(C) 60°

- (D) 160°.
- 48. The directivity of a broadside array of height 10  $\lambda$  and length 20  $\lambda$  is
  - (A) 34 dB

(B) 43 dB

(C) 53 dB

- (D) 35 dB.
- 49. Which of the following pulse modulation systems is analog?
  - (A) PWM

(B) PCM

(C) Delta

(D) Differential delta.

- 50. A signal is defined as x(t) = 4 tri(t). The value of  $x(\frac{1}{4})$  is
  - (A) 4

(B) 3

(C)  $\frac{1}{4}$ 

- (D)  $\frac{1}{3}$
- 51. An analog signal is sampled at 36 kHz and quantized into 256 levels. The time duration of a bit of the binary coded signal is
  - (A) 3·47 μs

(B) 2·77 μs

(C) 1·22 μs

- (D) 7.86 μs.
- 52. A coaxial cable having characteristic impedance of 50  $\Omega$  is to feed a half-wave dipole antenna of 75  $\Omega$ . The necessary matching load is
  - (A) 3·33 Ω

(B) 33·3 Ω

(C) 3·3 kΩ

- (D) 33 k $\Omega$ .
- 53. The range of firing in case of UJT triggering circuit is
  - (A) 0 90°

(B) 0 - 180°

(C) 0 - 270°

- (D) 0 360°.
- 54. The impulse response h [ n ] of a linear time invariant system is described by  $h[n] = e^{\alpha n} u[n] + e^{\beta n} u[-n]$  where u [ n ] denotes the unit step function and  $\alpha$  &  $\beta$  are constants. The system is stable if
  - (A)  $\alpha$  is positive &  $\beta$  is negative
  - (B)  $\alpha$  is negative &  $\beta$  is negative
  - (C)  $\alpha$  is positive &  $\beta$  is negative
  - (D)  $\alpha$  is negative &  $\beta$  is negative.

- 55. Which of the following is used to download a binary machine program from the development processor's memory into the target processor memory?
  - Device programmers
  - (B) **Emulators**
  - Debuggers (C)
  - Virtual machines.
- Scaling of channel length by  $\frac{1}{2}$  leads to
  - increase in channel resistance Ron (A)
  - decrease in channel resistance RON (B)
  - (C) no change in channel resistance RON
  - infinite value of channel resistance RON.
- Which one of the following is not embedded system characteristic? 57.
  - (A)
- Single functioned (B) Multi-functioned
- Tightly constrained (D) Reactive and real time.
- A thin dipole antenna is  $\frac{\lambda}{15}$ . If its loss resistance is 1.2  $\Omega$  then the efficiency is
  - (A) 41.1%

59% (B)

74.5% (C)

e

- 25.5%. (D)
- For a given data rate, the bandwidth required with m-ary transmission is smaller than 59. for binary transmission by
  - (A) log<sub>2</sub>m

(C) log<sub>2</sub>m

5000	)		26					I	13
60.		rms antenna current of an A. nodulated value. The modulation per			increas	ses by 2	0%	over	the
	(A)	25	(B)	93					
	(C)	47	(D)	16.					
61.	The	input impedance of a $\frac{\lambda}{8}$ long short	circuite	ed section		ssless trai			line
	(A)	zero	(B)	capacit	ive				
	(C)	inductive	(D)	infinity	a lannar	case in cl			
62.	Whi	ch of the following systems is linear '	?						
	(A)	ax [ n ] + b	(B)	$x^2[n]$					
	(C)	$x[n^2]$	(D)	$e^{x}[n]$ .	ot chan	nic value			
63.	Volt	age source inverter is used when		is not en					
	(A)	source inductance is small and load	l induc	tance is	large				
	(B)	source inductance is large and load	induct	ance is s	mall			(2)	
	(C)	source inductance is large and load	induct	ance is l	arge				
	(D)	source inductance is small and load	linduc	tance is	small.				
64.	Stat	ic current is high in							
	(A)	CMOS inverter	(B)	BiCMOS	S inverte				
	(C)	NMOS inverter	(D)			ite			
65.	The	impulse response of an LTI system is	s u (t).	The step	respon	se is			
	(A)	u(t)	(B)	δ(t)					

(D)

t.u(t).

(C)  $t.\delta(t)$ 

e

#### SECTION - II

Each question carries two marks.

Given the Z-transform pair 66.

$$3^n n^2 U[n] \stackrel{Z}{\longleftrightarrow} X[Z]$$

the time signal corresponding to  $X\left[Z^{-1}\right]$  is

- (A)  $n^2 3^{-n} U[n]$  (B)  $\frac{1}{n^2} 3^{-n} U[n]$
- (C)  $n^2 3^{-n} U[-n]$

(D)  $\frac{1}{n^2} 3^{\frac{1}{n}} U[-n].$ 

Electron transit time is directly proportional to ...... and inversely proportional 67. When 12 therefore are used in a string to withstand a D.C. vollage of W. a. 15.1 of

(A) length,  $V_{ds}$ 

 $V_{ds}, E_{ds}$ (B)

- (C) square of length,  $V_{ds}$
- (D)  $E_{ds}$ , length.

A DSB signal is generated using a square law modulator with characteristics 68.  $V_0 = A V_i + B V_i^3$ , the output of the non-linear device can be filtered by bandpass filter and the input signal  $V_i = m(t) + \cos(2\pi f_1 t)$ . What is the value of  $f_1$  if the carrier frequency of DSB generator is 1 MHz?

- speculation stenial with a resolution less than or equal to 50 Hz. The minimum
- (B) 0.5 MHz
- (C) 0.25 MHz

(D) 2 MHz. at hypoper legisla aplanta.

The antenna is desired to operate on a frequency of 30 MHz whose Q is 40. The 69. bandwidth of the antenna is

705 kHz (A)

(B) 750 kHz

750 Hz (C)

(D) 705 Hz.

(C) 17·89

5000	,	11.4	28		A 3
70.		ranges of resistance $R_1 \& R_2$ of = 20 V, $\eta$ = 0.66, $I_P$ = 10 $\mu$ A, $V_V$ = 2			neters :
	(A)	$15~\text{k}\Omega < R_1 < 10~\text{M}\Omega ~\&~757~\text{k}\Omega$			
	(B)	$5~\mathrm{k}\Omega < R_1 < 970~\mathrm{k}\Omega ~\&~7.57~\Omega$			
	(C)	100 Ω < $R_1$ < 6800 Ω & 75 7 kΩ			
	(D)	$1.75 \text{ k}\Omega < R_1 < 680 \text{ k}\Omega & 757 \Omega.$			
71.	and	sider voice transmission using BPS bandwidth efficiency of 1 bps/Hz. is increased to 19.2 kbps is			
	(A)	512	(B)	256	
estan,	(C)	128	(D)	8. Pythodo at and hand two.	
72.	the	en 12 thyristors are used in a string maximum steady state voltage shar e voltage derating factor is			
	(A)	37·5%	(B)	75%	
	(C)	25.15%	(D)	12%.	
73.	Drai	n current can be reduced	by	reducing ar	nd by
	(A)	L, W 1 to builty odd at health (1)	(B)	W, L III a langer transfer sets	
	(C)	$V_{ds}, W$	(D)	$V_{ds}, V_{gs}$ .	
74.	spec	$x_a(t)$ be an analog signal with battrum of signal with a resolution less halog signal record is			
	(A)	0.3 sec	(B)	0.03 sec	
	(C) -	0·2 sec	(D)	0.02 sec.	
75.		radiation resistance of an antenna is directivity if the power gain is 16?		and loss resistance is 8 $\Omega$ . What	will be
	(A)	17.78	(B)	17.87	

SPACE FOR ROUGH WORK

ANOW ROUGH ROY SCAN

(D) 17·98.

ıd

ly

by

th

be

#### PART - B

# (BME and ME : BIOMEDICAL ENGINEERING & MEDICAL ELECTRONICS)

#### SECTION - I

Each question carries one mark.  $20 \times 1 = 20$ 

- By definition, ultrasound is sonic energy at frequencies 46.
  - (A) > 20 kHz

(B) < 20 kHz

- (C) ≥ 20 kHz
- (D) ≤ 20 kHz.
- The density of water and most body fluids and tissues is approximately

  - (A)  $2.00 \text{ g/cm}^2$  (B)  $1.00 \text{ g/cm}^2$
  - (C)  $0.5 \text{ g/cm}^2$
- (D)  $0.25 \text{ g/cm}^2$ .
- The frequency range of X-ray is 48.
  - (A)  $10^8 \text{ MHz} 10^{10} \text{ MHz}$
- 10<sup>10</sup> MHz 10<sup>14</sup> MHz (B)
- (C)  $10^{12}$  MHz  $-10^{16}$  MHz
- $10^{14} \text{ MHz} 10^{18} \text{ MHz}.$ (D)
- 49. In order to visualize gastrointestinal tract during X-ray, barium sulphate is given orally because
  - (A) foreign bodies and bone absorb X-ray images readily than soft tissues
  - to increase X-ray absorption of intestinal tract than surrounding tissue (B)
  - (C) to make intestinal tract empty to enhance visualisation
  - (D). to provide different colours to the intestinal tract to enhance visualisation.
- In which imaging system mathematical reconstruction technique is used to visualise 50. detailed structures of an object?
  - X-ray image intensifier
- CT scanner (B)

(C) MRI system

Ultrasonic imaging system. (D)

		SPACE FOR ROUGH WORK
	(D)	EEG potential from a local region of the brain.
	(C)	pH of body fluids
	(B)	EMG potential from the surface of the skin
	(A)	bioelectric potential near within a single cell
56.	Glas	ss electrode is used to measure/record
	(C)	Laplace filter Mode filter. Mode filter.
	(A)	Mean filter Median filter Median filter
1		n image? The ment alther regent ver-X droeds and bus stabod agrard A
55.		ich of the following filters will in general have best performance in enhancing edg
		VK.L. transform. Fired ver z grand lost landestributing extensive of tobic of
	(C)	Hadamard transform W 104 2 (0)
	(B)	Walsh transform MIM 61 01 (8) AND WALL MAN WALL WALL MAN WALL WALL WALL WALL WALL WALL WALL WA
	(A)	Discerete cosine transform 2f var X to again your upon add
54.	The	transform used in JPEG image compression is
	(C)	Wavelet (D) Hadamard.
	(A)	Fourier deadxough at course but a (B) Hough thus to law to when the still
53.	The	transform that is effective in detecting lines in an image is
	(C)	17 Hz, 6 Hz (D) 25 Hz, 100 Hz.
	(A)	25 Hz, 50 Hz (B) 17 Hz, 50 Hz
		quency and a bandwidth of
52.		detect QRS complex, the ECG is passed through a bandpass filter with a cen
		remains constant I – MOI(D) 32 shifts by 5 units.
		increases by 5 (B) remains unchanged
51.	Wh	en a sequence is circularly shifted in time by 5 units, the magnitude response

31

A 3

5000

(D) linear convolution converted to circular convolution.

#### SECTION - II

(A) 500

(B) 1000

(C) 2000

(D) 4000.

her

20

:) t

Speech is digitized using a sampling rate of 8 kHz. An antialiasing filter with cut-off frequency of 3.4 kHz is preceded by sampler. The loss of speech signals in the frequency range 3.4 — 20 kHz due to antialiasing filter introduces a degradation in the signal quality. On the other hand, sampling without antialiasing filter also introduces degradation in the signal quality. Which of the following statements is true?

- (A) Degradation with antialiasing filter is less
- (B) Degradation without antialiasing filter is less
- (C) Degradation with or without antialiasing filter is the same
- (D) Degradation with antialiasing filter in the above frequency band is not much important.
- 68. The 2D DFT of the image  $\begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$  is
  - (A)  $\begin{bmatrix} 4 & 0 \\ 0 & 0 \end{bmatrix}$

 $\begin{bmatrix}
0 & 4 \\
0 & 0
\end{bmatrix}$ 

(C)  $\begin{bmatrix} 0 & 0 \\ 4 & 0 \end{bmatrix}$ 

- (D)  $\begin{bmatrix} 0 & 0 \\ 0 & 4 \end{bmatrix}$ .
- 69. The total number of bits required to represent a 256 ×256 image with 256 gray level is
  - (A) 524268

(B) 65536

(C) 16777216

- (D) 131072.
- 70. An ECG signal contains combination of base line drift, high frequency noise and power line and its harmonics interference. Which combination of filters are required?
  - (A) LP filter, HP filter and Notch filter
  - (B) LP filter and Comb filter
  - (C) LP filter, HP filter and Comb filter
  - (D) LP filter, HP filter and BR filter.

=	0	0	0	
Э	u	0	u	

Δ	-
473	62
	100

71.	<ol> <li>assigns variable length code words to a given quantized data saccording to their frequency of occurrence. Data that occur frequently are shorter code words.</li> </ol>								
	(A)	Huffman		(B)					
	(C)	Runlengt	h coding	(D)	AZTEC codi	ng. Mi man			
72.	The number of stages of FET computations required for the computation of DFT of 51 point sequence is								
	(A)	9	biline bill e	(B)	8				
	(C)	7		(D)	6.				
73.			following proper method ?	erties are true	for an IIR filt	er designed i			
		I) Requ	uires the use of	antialiasing filte	religion				
		II) Requ	uires prewrappir	ng the filter cut-	off frequencies				
		III) Not	suited for the de	sign of HP filter	S				
		IV) Resu	ılt in unique ma	pping from anal	log to digital fr	equencies.			
	(A)	I & II		(B)	I & III				
	(C)	II & III		(D)	II & IV.				
74.			of multiplication						
	(A)	256		(B)	120				
	(C)	128		· (D)	64.				
75.	(C) 128 (D) 64.  The residue method evaluates the residue of the function at poles that are								
	(A) outside the closed contour in the ROO			r in the ROC					
	(B)	anywhere	in ROC				다. (원)		
	(C) inside the closed contour in the ROC								
	(D)	outside th	ne ROC.				1 (0)		
1		4.1	SP	ACE FOR ROUGI	H WORK	/			

led

12

ear

two

A discrete time sugnet X (at ) is s B - TRAY an even and odd signal, it it sain

# (IT: INSTRUMENTATION TECHNOLOGY) SECTION - I

Each question carries one mark.

The numerical aperture of the fibre is expressed as 46.

- (A)  $(n_1 n_2)^{\frac{1}{2}}$  (B)  $(n_1^2 n_2^2)^{\frac{1}{2}}$

 $(n_2^2 - n_1^2)^{\frac{1}{2}}$ .

Linearity of a transducer is often specified in terms of 47.

- percentage of linearity
- percentage of non-linearity (B)
- (C) percentage of maximum error (D)
  - percentage of error.

Bioelectric potentials are generated due to difference in concentration of 48.

Na+, Cl- & K+ (A)

- Na<sup>+</sup>, Cl<sup>-</sup> & Mg<sup>+</sup> (B)
- Na<sup>+</sup>, Cl<sup>-</sup> & Ca<sup>+</sup>
- (D) Ca<sup>+</sup>, Mg<sup>+</sup> & Cl<sup>-</sup>.

49. Which of the following is called as the natural pacemaker of the heart?

- (A) AV node (B) Bundle of Nis
- SA node

(D) Purkinje fibres.

50. The CO<sub>2</sub> laser emits radiation at the wavelength of

1.06 um

(B) 325 nm

(C)  $2.36 - 3 \mu m$ 


(D) 10.6 µm.

51. Which of the following represents the impulse response of a system defined by  $H(z) = z^{-m} ?$ 

- u[n-m]
- $\delta[n-m] = \delta[n-m]$
- (C)  $\delta[m]$
- $\delta[m-n]$ .

x(t) or x(n) is defined to be a power signal, if and only if the average power content 52. of the signal is a/an

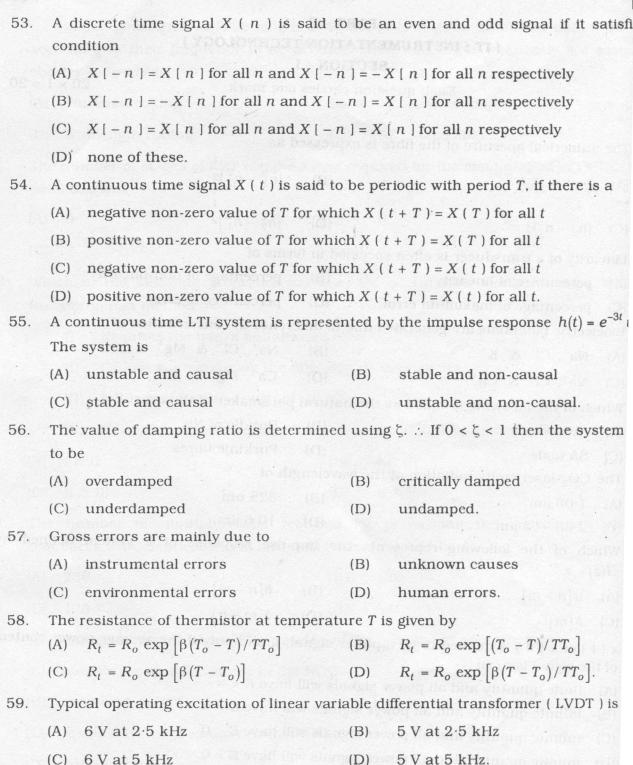- finite quantity and all power signals will have  $E = \infty$
- infinite quantity and all power signals will have  $E = \infty$
- infinite quantity and all power signals will have E = 0(C)
- infinite quantity and all power signals will have E = 0.



s the 60. Film Gamma of an X-ray film is expressed as

(A) 
$$\gamma = \frac{D_1 - D_2}{\log_{10} E_2 - \log_{10} E_1}$$

(B) 
$$\gamma = \frac{D_1 - D_2}{\log_{10} E_1 - \log_{10} E_2}$$


(A) 
$$\gamma = \frac{D_1 - D_2}{\log_{10} E_2 - \log_{10} E_1}$$
(C) 
$$\gamma = \frac{D_2 - D_1}{\log_{10} E_2 - \log_{10} E_1}$$

(D) 
$$\gamma = \frac{D_2 - D_1}{\log_{10} E_1 - \log_{10} E_2}$$

Blood gas analysers are designed to measure 61.

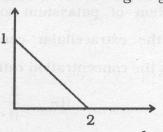(D) pH, 
$$pCO_2$$
 and  $pO_2$ .

Identify the correct Laplace transform for the signal given in figure : 62.



(t-1).


(A) 
$$\frac{1}{T_2^2} \left[ 1 - e^{-TS} \left( 1 + TS \right) \right]$$

(B) 
$$\frac{1}{T_2^2} \left[ e^{-TS} \left( 1 + TS \right) \right]$$

(C) 
$$\frac{1}{T_2^2} \left[ e^{-TS} + (1 - TS) \right]$$

(C) 
$$\frac{1}{T_2^2} \left[ e^{-TS} + (1 - TS) \right]$$
 (D)  $\frac{1}{T_2^2} \left[ 1 - e^{-TS} + TS \right]$ .

The function of the following circuit is

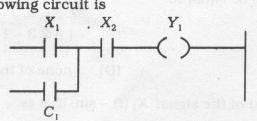

(A) 
$$Y_1 = (X_1 \text{ OR } C_1) \text{ AND } X_2$$

(B) 
$$Y_1 = (X_1 \text{ OR (NOT } C_1)) \text{ AND } X_2$$

(C) 
$$Y_1 = (X_1 \text{ AND } X_2) \text{ OR } C_1$$

(D) 
$$Y_1 = (X_1 \text{ AND } X_2) \text{ OR (NOT } C_1).$$

The transfer function of Tachometer is of the form 64.

(B) 
$$\frac{K}{S}$$

(C) 
$$\frac{K}{(S+1)}$$

(D) 
$$\frac{K}{S(S+1)}.$$

The thermocouple used for temperature measurement may have 65.

(A) only one junction

(B) two junctions

(C) 2 to 20 junctions

(D) no junction.

### SECTION - II

Each question carries two marks.

 $10 \times 2 = 20$ 

- 66. What is the output voltage of a transducer which has the excitation potential of 5 V D.C, applied force 15 g and a sensitivity of 10  $\mu$  V/V-g?
  - (A) 750 mV

(B) 750 μV

(C) 7.5 V

- (D) 75 V.
- 67. The intracellular concentration of potassium ions in a group of cells averages  $150\times10^{-6}~\text{moles/cm}^3$  and the extracellular concentration of potassium averages  $6\times10^{-6}~\text{moles/cm}^3$ . What is the concentration ratio?
  - (A)  $\frac{1}{4}$

(B)  $\frac{2}{6}$ 

- (C)  $\frac{1}{8}$
- $\left[ (27+1)^{\frac{27}{57}} s \right] \frac{1}{\frac{1}{57}} \qquad (8) \quad (D) \qquad \frac{2}{5}. \qquad \left[ (27+1)^{\frac{27}{57}} s 1 \right] \frac{1}{\frac{1}{57}}$
- 68. Let two signals be  $X_1(n) = \begin{bmatrix} 1 & 2 & -1 & 2 \end{bmatrix}$  and  $X_2(n) = \begin{bmatrix} -2 & 1 & 3 & 1 \end{bmatrix}$  and the addition of these two signals Y(n) be equal to
  - (A) [-1323]

(B) [323-1]

(C) [3-132]

- (D) none of these.
- 69. The fundamental period of the signal  $X_1(t) = \sin 15\pi t$  is
  - (A) 0·13333 second

(B) 1.3333 seconds

(C) 13·333 seconds

- (D) 0.013333 second.
- 70. The equation for critical damping is
  - (A)  $B = x(0) + \omega_0 x(0)$

- (B)  $B = \frac{-\gamma + x(0) x(0)}{\gamma -\gamma + }$
- (C)  $B = \frac{1}{\omega d} \left( \zeta \omega_0 x(0) + \dot{x}(0) \right)$
- (D) none of these.

0

V

S

S

71.  $f_1(t) = 4$  for 0 < t < 2

= 0, otherwise

 $f_2(t) = u(t-1)$  the convolution is  $f = f_1 \times f_2$ . The value of  $f_3(t)$  is

(A) 0

(B)

(C) 8

(D) 12.

A resistance strain gauge has a gauge factor of 2. The change in resistance  $\Delta R$ , of the 72. strain gauge element due to applied stress ( Assume strain (  $\sigma$  ) =  $5\times10^{-4}\,$  ) is

(A) 0.001%

(B) 0.01%

(C) 0·1%

(D) 1%.

A system described by state equation  $X^1 = AX + BU$ . The O/P is given by Y = CX where  $A = \begin{bmatrix} -4 & -1 \\ 3 & -1 \end{bmatrix}, B = \begin{bmatrix} 1 \\ 1 \end{bmatrix}, C = \begin{bmatrix} 1 & 0 \end{bmatrix}$ . Transfer function (TF) G(S) of system is

 $(A) \quad \frac{S}{S^2 + 5S + 7}$ 

(C)  $\frac{S}{S^2 + 3S + 3S}$ 

(B)  $\frac{1}{S^2 + 5S + 7}$ (D)  $\frac{1}{S^2 + 3S + 2}$ 

Let X(n) = n;  $-3 \le n \le 3$ . The folded signal of X(n) will be equal to 74.

- (A)  $X_1(n) = -X(-n) = n; -3 \le n \le 3$
- (B)  $X_1(n) = X(-n) = -n + 1; -3 \le n \le 3$
- (C)  $X_1(n) = X(-n) = -n 1; -3 \le n \le 3$
- (D)  $X_1(n) = X(-n) = -n; -3 \le n \le 3.$

The impulse response of an LTI system is  $e^{-2t}$ . If the input is a unit step with system 75. initially at rest, the response is given by

(A)  $1 - e^{-2t}$ 

(B)  $\frac{1}{2} - \frac{1}{2}e^{-2t}$ 

(C)  $\frac{1}{2} + \frac{1}{2}e^{-2t}$ 

(D)  $-2e^{-2t}$ .