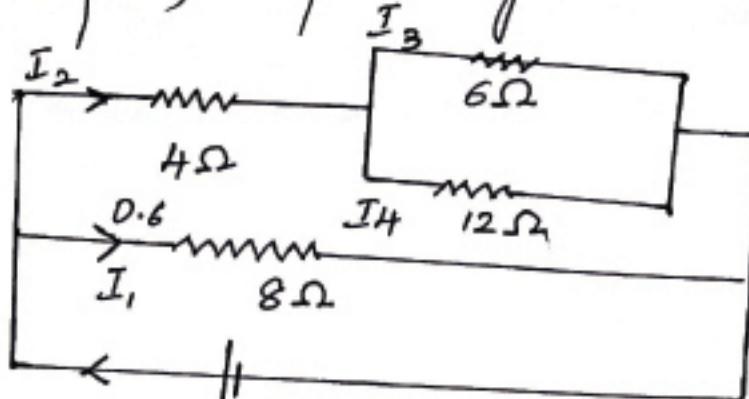


1] In the given circuit, values of I, I_1, I_2, I_3 & I_4 are (in Ampere) respectively.




- a) $1.2, 0.6, 0.6, 0.4, 0.2$. b) $1.2, 0.6, 0.6, 0.2, 0.4$.
- c) $1.5, 0.8, 0.7, 0.3, 0.4$. d) $1.5, 0.6, 0.9, 0.4, 0.5$.

2]. The uniform wire of resistance r m
is bent into a circle and two points
at a quarter of circumference apart are
connected to a battery of Emf $2.3V$, ($r=4$)
then I_1 & I_2 are


- a) $0.6A, 0.2A$. b) $0.2A, 0.6A$.
- c) $0.3A, 0.1A$. d) $0.1A, 0.3A$.

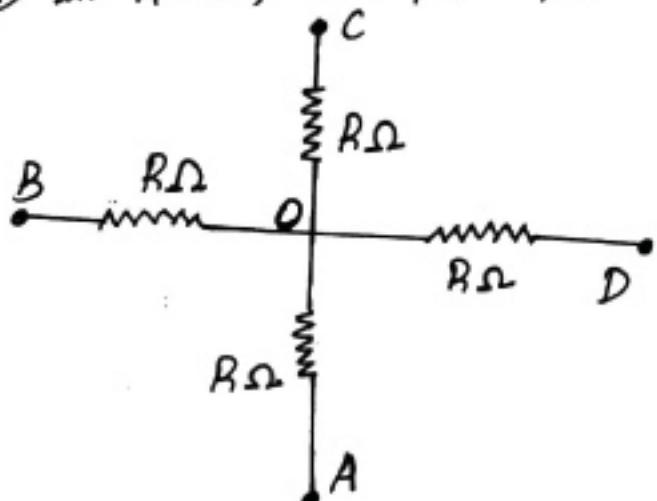3) The given 4-terminal N/W is the part of a larger circuit, the points A, B, C are at same potential, the potential difference b/w any one of the points are A or B or C and D is 40 V, the pd b/w A & 0.



- a) 10V
- b) 15V
- c) 18V
- d) 20V.

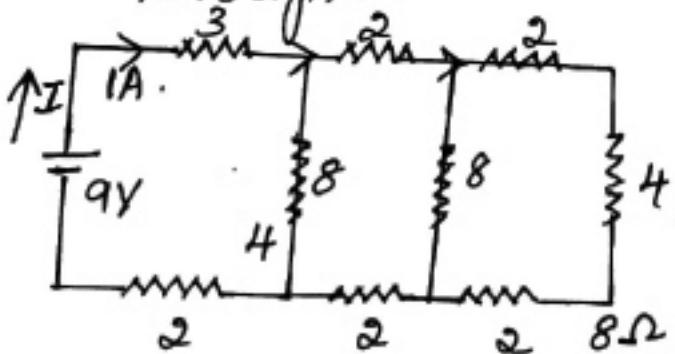4) In the circuit shown in figure the Current through



- a) 3Ω resistor is 0.5A.
- b) 3Ω resistor is 0.5A
- c) 4Ω resistor is 0.5A.
- d) 4Ω resistor is 0.25A.


5) A housewife uses 100 W bulb, 8 hours a day & an electrical heater of 300 W for 4 hours a day total cost for the June month at ₹. 1 per unit is.

- a) 20
- b) 120
- c) 30
- d) 60.

6) A wire when connected across 220V mains has power dissipated P_1 , now the wire is cut into two equal pieces which are connected in parallel to same, power dissipated in this case is P_2 then $P_2:P_1$ is.

- a) 1
- b) 2
- c) 3
- d) 4.

7) If Diode's have forward resistance of

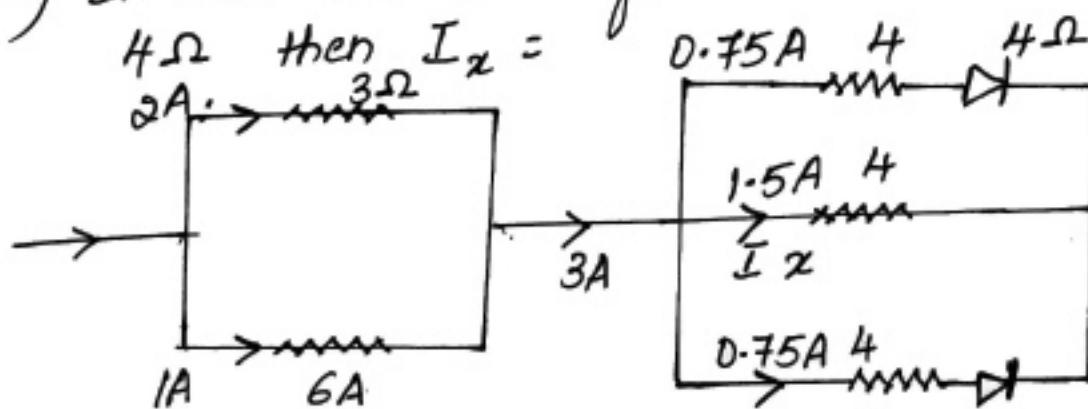

- a) 1.5A
- b) 2A .
- c) 3A
- d) 1A.

8) Masses of 3 Cu wires are in the ratio 1:3:5 and lengths are in the ratio 5:3:1 ratio of their electrical resistance is.

- a) 1:3:5 b) 5:3:1 c) 1:15:125 d) 125:15:1

Key Answers .

1] a	2] a	3] a
4] d	5] d	6] d
7] a	8] d	