

CURRENT ELECTRICITY

1. Ans: the force due to electric field = qE

Force due to magnetic field = $qvB\sin\theta$ $\theta=0$

i.e. magnetic field does not exert any force. but the particle experience a force due to electric field and gains velocity. So the particle will move in the direction of the electric field along a straight line

.Answer: (1)

2. In mechanics momentum $p = mv = mdr/dt$

Similarly $LI = Ldq/dt$ is analogous to momentum.

Answer is (1).

3. Ans: upward. Applying Fleming's left hand thumb rule, if forefinger is set in the direction of field direction (south), middle finger along direction of proton (eastward), thumb points in the downward direction towards which proton is deflected.

Answer: (2)

4. Answer $F = Bqv$ and $B = F/qv = MLT^{-2}/CLT^{-1}$

$[B] = MT^{-1}C^{-1}$ answer : (1)

5. Ans: since the charged particle enters perpendicular to magnetic field, it describes circular path. Since velocity and force are mutually perpendicular, no change in the velocity. Hence both momentum and kinetic energy remains constant. Answer: (2)

6. $r = mv/Bq$
 therefore $r \propto m/q$
 ram

7. if I_2 is the current through voltmeter branch, and R = resistance of the voltmeter,
 Then $V = I_2 R$ $120 = (IR_1/R + R_1)R$
 $120 = (2 \times 75/75 + R)R$ OR $120 = 150R/75 + R$
 or $75 + R = 150R/120$

On solving we get $R = 300$ ohm . Answer : (3).

8. we know that in parallel combination,
 maximum current flows along the least resistance
 .so $I_1/I_2 = R_2/R_1 = I_2/A_2 \times A_1/I_1 = I_2/I_1 \times A_1/A_2 = \frac{3}{4} \times \frac{2^2}{3^2}$
 $= \frac{3}{4} \times \frac{4}{9} = \frac{1}{3}$. Therefore answer is (2)

9. we know that ,magnetic field at the centre of a
 circular coil is $B = \frac{Kn}{r}$.if the coil is rewound to
 have 'n' turns, radius decreases by 'n' times .B is
 proportional to n/r

$$B'/B = \frac{n/r}{r/n} = n^2$$

$B' = n^2 B$.answer is (2)

10. The initial force is given by $F = kI_1 I_2 / d$
 .when current in one of them is doubled and
 distance becomes $3d$, the force becomes
 $F' = k2I_1 I_2 / 3d$. $F'/F = 2/3$ but nature of the force is also
 reversed. Hence the answer is $F' = -2/3F$.Ans : (1)

11. shunt resistance required is given by
 $S = I_g G / I - I_g$.here, $I_g = 1A$, $G = 0.81$ ohm and $I = 10A$
 Substituting we get
 $S = 1 \times 0.81 / 10 - 1 = 0.81 / 9 = 0.09$ ohm

Answer is (3)

12. When length of a wire is decreased 4 times, area of cross-section increases by 4 times. therefore

$$R_2/R_1 = l_2/A_2 \times A_1/l_1 = l_1/4/4A_1 \times = 1/16$$

Answer:(3)

13. When two cells are parallel. The effective potential difference of the combination is given by (when they send the current in the same direction)

$$\begin{aligned} V &= E_1 r_2 + E_2 r_1 / r_1 + r_2 \\ &= 18 \times 1 + 12 \times 2 / 2 + 1 \\ &= 18 + 24/3 = 42/3 = 14V \end{aligned}$$

Hence answer is (4)

14. current in a circuit is inversely proportional to the resistance. Let 'R' is the initial resistance. If another resistance of 3Ω is connected in series to R, effective resistance is $R+3$. Then current becomes $2A$ $I_2/I_1 = R_1/R_2$

$$2/5 = R/R+3 \quad 2R+6=5R \quad 3R=6 \quad R=2\text{ohm} \quad \text{Answer is (3).}$$

15. If resistance $R\Omega$ is cut into 20 pieces, then resistance of each part becomes $R/20$. If half of the pieces i.e. 10 pieces are joined in series. $R_s = 10(R/20) = R/2$. other 10 pieces are joined in parallel. Since $R_p = R/n = (R/20)/10 = R/200$

**If $R/2$ and $R/200$ are connected in series again, the effective resistance is $R_s = (R/2) + (R/200)$
 $= 100R + R/200 = 101R/200$. answer is (3)**

16. If length of the 2Ω wire is doubled, the new resistance is $R_2 = n^2 R_1 = 2^2 \times 2 = 4 \times 2 = 8\Omega$. If 8Ω

is bent in the form of a circle, resistance of each quarter part is 2Ω .

Because $1/4$ the circumference is considered, longer arc of 6Ω and 2Ω are parallel. Then effective resistance is R_p

$$= R_1 R_2 / R_1 + R_2 = 6 \times 2 / 6 + 2 = 12 / 8 = 3 / 2 = 1.5 \text{ ohm.}$$

Hence answer is (4).

17. we know that the magnetic moment of a current loop is $M = IA$. Equivalent current due to revolution of electron is $I = e/T = e/2\pi r/v = ev/2\pi r$. but $A = \pi r^2$.

$$\text{Therefore } M = (ev/2\pi r) \times \pi r^2 = 1.6 \times 10^{-19} \times 5 \times 10^{11} \times 2 \times 10^6 / 2 = 8 \times 10^{-24} \text{ Am}^2. \text{ answer is (3)}$$

18. the current in the circuit containing capacitor is given $I = V/X_C$ given $V_0 = 200 \times 2^{1/2} \text{ v.}$

$$X_C = 1 / 100 \times 10 \times 10^{-6} = 1000 \text{ ohm.}$$

$$I_0 = 200 \times \sqrt{2} / 1000 = 200 \sqrt{2} \text{ mA.}$$

But ammeter reads rms value of current.

therefore $I_{\text{RMS}} = 200 \times \sqrt{2} / \sqrt{2} = 0.02 \text{ A} = 20 \text{ mA.}$ Hence answer is (2)

19. Resistance of the coil $= R = 10 \Omega$ and phase angle $= 45^\circ$ But phase angle is given by

$$\tan 45^\circ = X_L / R \quad \text{OR } X_L = R = 10 \Omega$$

$$\text{i.e. } 2\pi fL = 10 \text{ or } 2 \times 3.14 \times 100 \times f = 10 \text{ or } f = 10 / 628 = 0.01599 = 16 \text{ mH. Answer : (3)}$$

20. the power in an ac circuit is $P = V_{\text{rms}} I_{\text{rms}} \cos 60^\circ$.

$$V_0 = 100 \text{ V and } I_0 = 100 \times 10^{-3} \text{ A so}$$

$$P = (100 \times 100 \times 10^{-3} / 2) \times 1/2$$

$$= 50 \times 50 \times 10^{-3} = 2.5 \text{ W. answer is (3)}$$

21. the power dissipated in a resistor is $P=V^2/R$
since resistance of the wire is assumed to be
constant $P_2/P_1 = V_2^2 / V_1^2$

$$P_2 = 500(15 \times 15 / 100) = 1125W$$

22. heat required to melt 'm' kg of ice = $Q = mL$

$L =$ latent heat of fusion

Heat produced in the resistor $H = VIt$.

$mL = VIt$

$$m = VIt/L = 210 \times 1 \times 3600 / 3.6 \times 10^5$$

$$= 2.1 \text{ kg .Answer : (2)}$$

23. resistance of a wire is given by $R = kl/A$ $R = kl/r^2$

$$R_2 / R_1 = r_1^2 / r_2^2 \quad R_2 = 5 \times 9^2 / 3^2 = 5 \times 81 / 9 = 45\Omega$$

If such six wires each of 45Ω is connected in
parallel, $R_p = 45/6 = 7.5\Omega$

24. given rating of the bulb is $90W-30V$. using

$$R = v^2/P = 30 \times 30 / 90 = 10\Omega$$

Also current needed by the bulb to glow with
maximum intensity is calculated by
 $I = P/V = 90/30 = 3A$. If the bulb is connected with
another resistance of $X\Omega$, then current in the circuit
is equal to $I = E/R + X$ or $3 = 120/10 + X$ or $10 + X = 40$
therefore $X = 30\Omega$..answer is (3)

25. when a wire is stretched n times resistance new
resistance = $n^2 \times$ initial resistance. after stretching
resistance of the wire is $R = 2^2 \times 3 = 4 \times 3 = 12\Omega$

If it connected to form a triangle two arms of the
triangle are in series and third side is in parallel with
it. Therefore 8Ω parallel to 4Ω . $R_p = 8 \times 4 / 8 + 4 = 32/12$
 $= 8/3$ Answer :(2)

26. the force experienced by an electron in the electric field is $F=eE$

But $E=F/e$, V being the P.d.across the wire = EMF of the cell equating ,we get

$$F=ev/l$$

$3.2 \times 10^{-19} = 1.6 \times 10^{-19} \times V/4$ solving this we get $V =$
emf of the battery =8V . The answer is (4)

27.we know that low wattage bulb will have high resistance.(since $R=v^2/P$) Heat produced is $H=I^2Rt$ i.e. hence 25W bulb glows more brightly when they are in series. the answer is (1)

28. shunt resistance is calculated by $S=I_g G/I-I_g$
her $G=R$ and $I_g =I$. $S=IR/4I-I =R/3$.
therefore the answer is (1)

29.since particles have same charge and accelerated through same p.d. their kinetic energies are equal. We have
therefore $v=BqR/m$ $mv^2/R=Bqv$
 $KE=1/2(mv^2)=1/2 m[B^2q^2R^2/m^2] =1/2[B^2q^2R^2/m]$ Since
kinetic energies
are equal $R_1^2/R_2^2=m_1/m_2$ or $m_1/m_2=[R_1/R_2]^2$
answer is (4)

30.using Flemings left hand thumb rule , electron experiences a force in upward direction.
hence answer is (1)

31. we know that shunt resistance is given by
 $S=I_g G/I-I_g$ Given $I_g=0.02I$

therefore $S = 0.02IG/l - 0.02I$
 $= 0.02G/0.98 = G/49$
hence answer is (2).

32. induced emf = -rate of change of magnetic flux
 $e = -d/dt(BA) = B \times dA/dt$
 $= -3.14 \times 0.02 \times (2 \times 0.04) \times (-10^{-3})$
 $= 5 \times 10^{-6} = 5 \mu V$. Hence answer is (3)

33. since current is divided equally into two parts and flows in opposite direction, each part produces equal and opposite magnetic field at the centre of the loop. hence resultant magnetic field is zero. Therefore the answer is (1)

34. magnetic moment of a coil = iA
 $= i(\pi r^2)$
Given that $2\pi r = L$ or $r = L/2\pi$ $M = iL^2/4\pi$
Answer :(1)

35. on inserting the iron rod into the coil, the inductive reactive (X_L) increases. Hence impedance of the circuit also increases. which results in decrease of current. hence intensity of the bulb decreases. Correct answer is (1).

36. if a wire is stretched by $n\%$, resistance increases by $2n\%$. therefore, if length is increased by 10% , resistance increases by 20% . New resistance is $R = 10\Omega + 20\% \text{ of } 10\Omega = 10 + 2 = 12\Omega$. therefore answer is (3)

37. $P/Q = 400/X$ $Q/P = 441/X$

solving these two $X = \sqrt{400 \times 441} = 20 \times 21 = 420 \Omega$.

38. because one of the cells is reversed, it nullifies emf of one cell.

$$\text{Total emf} = 1.5 + 1.5 = 3V$$

$$\text{Total internal resistance of four cells} = 4 \times 1/4 = 1 \Omega$$

$$\text{Therefore current in the circuit is } I = 3 / (1 + 1) = 3/2 = 1.5 \text{ A}$$

Therefore answer is (4)

39. we have to find the main current = current through 4 ohm = I

$$\text{We know that branch current } I_1 = I \times R_2 / (R_1 + R_2)$$

$$0.8 = I \times 6 / (6 + 3) \text{ or } 0.8 = 2I/3 = 1.2A$$

$$\text{hence p.d. across } 4 \Omega = IR$$

$$= 1.2 \times 4 = 4.8 \text{ V}$$

40. the heat dissipated in a resistor is

$$Q = I^2 R$$

$$80 = 2^2 \times R \times 10$$

$$8 = 4R \quad R = 2 \Omega \quad \text{Answer is (2)}$$

41. 500 ohms in parallel with 500 ohm.

$$\text{So } R_p = R_1 R_2 / (R_1 + R_2) = 250 \text{ Ohm.}$$

This is series with remaining part of the rheostat.

$$\text{Their eff. res} = 500 + 250 \text{ ohm}$$

$$\text{Current in the ckt } I = E/R \quad I = 15/750A$$

$$\text{Branches are equal - } I_1 = I_2 = 1/2 [15/750]$$

$$\text{AMMETER READING} = 15/1500 = 0.01A$$

Answer (c)

42. each branch contain same resistance i.e (p+q)

$$\text{Current divides equally } I_1 = I_2 = 1A$$

$$\text{P.d. across } p = I \times p = P \text{ volts}$$

P.d. across Q = $1 \times Q = Q$ volts
Then p.d. = $V_A - V_B = P - Q$

43. Resistance of the bulb = $V^2/p = 1.5 \times 1.5 / 4.5 = 0.5 \text{ Ohm}$
 $R_p = 1 \times 0.5 / 1 + 0.5 = 1/3 = 0.333 \text{ ohm}$
Current required for its glow = $I = P/v = 4.5 / 1.5 = 3 \text{ A}$
Similarly current in ohm branch = $I = V/R = 1.5 \text{ A}$. Wkt
 $I = E / R_p + r$
 $(3 + 1.5) = E / 1.333 + 2.67$ $4.5 = E/3$ $E = 13.5 \text{ V}$

44. emf = amount of work done to transfer 1 coulomb of charge
charge transferred $Q = It = 2 \times 6 \times 360 \text{ coulombs}$
To transfer Q, work done = 1000 J
to transfer work done = emf = $1000 / (2 \times 6 \times 360) = 2.03 \text{ j}$
therefore $E = 2.03$

45. The voltage across the cell
= terminal p.d
= $E - Ir$
= $E - (E/R + r)r$
= $2 - [2 \times 0.1 / 3.9 + 0.1]$
= $2 - [0.2/4]$
= $2 - 0.05 = 1.95 \text{ V}$. Answer : (3)

46. $E = i(R + r)$
 $E = 0.5 \times (r + 2) = 0.25 \times (r + 5)$
Therefore $r = 1$
and $E = 1.5 \text{ V}$. Answer: (3)

47. Hint: $R_2 / R_1 = (l_2 / l_1) \times (A_1 / A_2)$ if radius decreases by $1/3$.
Area of cross-section by $1/9$. Therefore length

increases 9 times. Answer: (3) 81:1

$$8. P = I^2 R = \frac{E^2}{R + R}^2$$

$$150 = E^2 \times 6 / (6 + r)^2$$

$$196 = E^2 \times 4 / (4 + r)^2 \text{ solving, we get}$$

$$r = 1 \Omega$$

49. current flowing through the voltmeter

$$= I = V/R = 200 / 20 \times 10^3$$

$$= 10 \times 10^{-3}$$

same current flows through R

$$\text{then } R = 30 / 10 \times 10^{-3} = 3 \text{ k}\Omega$$

$$50. I_1 = v/R_1 \quad 1 = V/R_1 \quad R_1 = v$$

$$I_2 = V/R_2 \quad 3 = V/R_2 \quad R_2 = V/3$$

$$I_3 = V/R_3 \quad 6 = V/R_3 \quad R_3 = v/6$$

$$R_s = V + V/3 + V/6 = 9/6 V$$

$$I = V/R_s = V / (9/6) V = 2/3 V$$

51. resistance is least when they are connected in parallel. When all the six of them are in parallel, effective resistance will be

$$R_p = R/6 = 0.6/6 = 0.1 \Omega$$

52. It is known that current is independent of area of

cross-section. therefore is (4)

$$53. \text{ WKT } R_s = nR \quad R_p = R/n$$

$$X = nR \quad Y = R/n$$

$$XY = R^2 \text{ .therefore } R = \sqrt{XY}$$

54. Since all the bulbs should get 200V, they are in

parallel. Resistance of each bulb
 $=R=V^2/p=200 \times 200/100=400 \Omega$
 There fore $I=E/R_p$
 $5=200/(400/n)$
 $5=200n/400$.solving we get $n=10$.

55.Internal resistance of the battery can be calculated as follows $I=E/R+r$
 $1=4/2+r$ OR $2+r=4$
 $r=2 \Omega$
 when terminals are connected directly $R=0$
 $I=E/r =4/2=2A$

56.Effective resistance of the network= $20/7 \Omega$
 Therefore main current $I=E/R=2[20/7] =7/10A$
 Current through each branch= $1/10A$. since four branch currents pass through ammeter,
 reading= $4/10A$

57.Pot.gradient
 $V/L=IR/L=[I/L] \times [\rho L/A]$
 Therefore $V/L=I\rho/A$

58.given $R_p=R_1R_2/R_1+R_2$ $R_p=1.2 \Omega$ and one the resistanc = 2Ω
 $1.2=2R/2+R$
 $2.4+1.2R=2R$
 $2.4=2R-1.2R$
 $2.4=0.8R$ solving we get $R=3 \Omega$

59. $Bev=mv^2/r$
 $B=mv/er$ but $v=2\pi r/T$
 $B=[m/er] \times [2\pi r/T]$

$$\begin{aligned}
 B &= \frac{m \times 2\pi}{eT} \\
 &= \frac{(9.1 \times 10^{-31} \times 2 \times 3.14)}{(1.6 \times 10^{-19} \times 1 \times 10^{-6})} \\
 &= 3.6 \times 10^{-5} \text{ T}
 \end{aligned}$$

60. Magnetic field due to a straight conductor is

$$\begin{aligned}
 B &= \frac{\mu_0 I}{2\pi d} \\
 B &= \frac{4\pi \times 10^{-7} \times 90}{2\pi \times 1.5} \\
 B &= 1.2 \times 10^{-5} \text{ T}
 \end{aligned}$$

61. Force acting on a current carrying conductor due to magnetic field = BIL

Weight of the wire = $w = mg$

To support $F = W$

$$\begin{aligned}
 BIL &= mg \quad B = mg/IL \\
 B &= \frac{3 \times 10^{-4} \times 9.8}{5 \times 1} \\
 B &= 0.6 \times 10^{-3} \text{ T}
 \end{aligned}$$

62. $e = d\phi/dt$

$$|d\phi| = e \times dt$$

$$= V \times T$$

$$= J/C \times T \quad I = Q/T \quad |Q| = |It| = AT$$

$$= F \times S \times T/AT$$

$$= MLT^{-2}LXT/AXT$$

$$= ML^2T^{-2}A^{-1}$$

63. P.d. across voltmeter = 5V

Res. of the voltmeter = $20 \times 10^3 \Omega$.

Current through voltmeter = $V/R = 5/(20 \times 10^3)$

Same current flows through resistance R. potential difference across resistor = $110 - 5 = 105V$

$$R = V/I = 105 / \left(\frac{5}{20 \times 10^3} \right) = 420 \Omega$$

64. at resonance , inductive reactance = capacitive reactive . hence $Z=R$. so voltage is always in phase with current.

65. the rms value of Ac= the current which produces same heat as the dc current . therefore $20\sqrt{2}$ amperes of dc current produces same heat as produced by 20A of ac

66. on heating a conducting wire its resistance increases. since R is proportional to length, to keep the balance again, the balancing point shifts toward right.

67. since radius of the circle is proportional to mass. Radius of proton path is greater than that of electron. hence time period of proton is more than that of electron

68. Hint : at each end face of the coil, magnetic poles are created . depending on the direction of the current since opposite poles are created in the two loops facing each other, they attract and spring contracts

69. electrostatic force

$$F_e = (1/4\pi\epsilon_0) e^2/r^2$$

Magnetic force

$$F_m = \mu_0/\pi [e^2 v^2/r]$$

Deviding one by the other,

$$F_m/F_e = \mu_0 \epsilon_0 v^2 = v^2/c^2$$

(since $\mu_0 \epsilon_0 = 1/c^2$)

70. Hint. Magnetic field intensity is stronger near the poles. Hence change in the magnetic flux is higher. more emf may be induced

71. since $X_L = 2\pi fL$, X_L increases.
 $X_C = 1/2\pi fC$, X_C decreases.
Hence $Z = \sqrt{R^2 + [X_L - X_C]^2}$ increases

72. using Fleming's left hand thumb rule.
fore finger - towards east
Middle finger - towards south
Then Thumb is set - vertically downwards
(2)

73. wkt $B = mv/er$ since momentum (mv) for both proton and electron is same, r is also same.
Hence answer is (3)

74. $qvB = qE$
 $2 \times 10^3 \times 1.5 = E = 3 \times 10^3 \text{ N/C}$

75.
 $qvB = mv^2/r$
 $v = qBr/m = \omega r = 2\pi fr$
or $f = qB/2\pi r$

76.
 $V = i_g G$
 $nV = i_g (G + R)$
or $1/n = G/G + R$
or $G + R = nG$
or $R = (n - 1)G$

77.

$$r = mv/qB$$

$$A = \pi r^2$$

$$= \pi (mv)^2 / q^2 B^2$$

$$= \pi \cdot 2mE / q^2 B^2$$

therefore area is proportional to energy

78. $V^2 = V_R^2 + (V_L - V_C)^2$

$$V^2 = 40^2 + (60 - 30)^2$$

$$V^2 = 40^2 + (30)^2$$

$$V^2 = 50^2$$

$$V = 50V$$

79. we know that $f = 1/2\pi\sqrt{LC}$

When C is doubled, L should be halved so that resonant frequency remains unchanged

80 .The radius of curvature of a charged particle moving in the magnetic field is given by

$$r = mv/qB = \sqrt{2mK}/qB$$

$$r' = \sqrt{2mK'}/qB$$

$$r'/r = \sqrt{K'/K} = \sqrt{k/2/k} = 1/\sqrt{2}$$

therefore $r' = 1/\sqrt{2}r$

81. deflection becomes half if current reduced by half .that means resistance of the shunt must be equal to resistance of the galvanometer so that the current divides equally.

82,. Radius of curvature r of the path of the charged particle is given by $r = mv/qB$

Where m is the mass, v be its velocity. when q and B are fixed, then r is proportional to mv (momentum of the particle)

83. Principle: a cell delivers maximum current when external resistance = internal resistance .
(Maximum power transfer theorem)

84. low wattage bulb has high resistance.
Powers are in the ratio 1:4 therefore $R_2/R_1=1/4$ Then
p.d. are in the ratio $V_1/V_2=4$
But $V_1+V_2=440$. On solving we get
p.d. across 25W bulb = 352V
p.d. across 100W bulb = 88V
Since p.d. across 25W bulb is more than tolerance. It will fuse

85. on completing half revolution, the force vector and velocity are mutually perpendicular. hence work done by the magnetic field is zero. Hence there is no increase in the kinetic energy

86. Equation for the self inductance of a coil is
 $L = \mu_0 N^2 A / l$
Therefore if number of turns is doubled, L increases four times

87. Given $I_0 = 50\sqrt{2}$
Therefore $I_{rms} = I_0 / \sqrt{2}$
Or $I_{rms} = 50A$
Also $2\pi f = 400\pi$
 $f = 200Hz$

88. We know that $V=IR$

$$V=(neAv_d)\rho L/A$$

Therefore if V is doubled, drift velocity also gets doubled.

89. slope of VI graph gives resistance which is proportional to temperature. there slope $\tan\theta$ proportional to T_1

$\tan(90-\theta)$ proportional to T_2

$$T_2 - T_1 = \cot\theta - \tan\theta$$

$$= \cos\theta/\sin\theta - \sin\theta/\cos\theta$$

$$= \frac{\cos^2\theta - \sin^2\theta}{\sin\theta \cos\theta}$$

$$= \text{proportional to } \cot\theta$$

90. when electron approaches the loop, the downward flux linked with the coil increases. so anticlockwise current is induced in the loop. when electron recedes away from the loop, downward flux decreases. so clockwise current is induced in the loop.

91. we angular frequency $\omega=2\pi f$

$$= 2\pi \times [1/2\pi \sqrt{LC}]$$

$$= 1/\sqrt{LC}$$

substituting the value of L and C we get

$$\omega = 1 \times 10^4$$

92. HINT

$$I = q/t = e/T = fe = 1.6 \times 10^{-19} \times 5 \times 10^{10}$$

$$= 8 \times 10^{-4} = 8 \text{mA}$$

93Ans: we know that

$$I_1/I_2 = \tan\theta_1/\tan\theta_2$$

$$2/I_2 = \tan 30^\circ / \tan 60^\circ$$

$$2/I_2 = 1/3$$

$$\text{therefore } I_2 = 6\text{A}$$

$$94.\text{Ans: impedance } Z = \sqrt{R^2 + X^2} = \sqrt{3^2 + 4^2} = 5\Omega$$

$$\text{Power factor } \cos \phi = 3/5 = 0.6$$

$$95.\text{we know that } \tan \phi = X_L/R$$

$$\tan 45^\circ = X_L/R$$

$$\text{Therefore } X_L = R$$

96. The coils are connected in series. Hence irrespective of the magnetic fluxes, the inductances are added in series combination. Hence resultant inductance is $L+L=2L$

$$97. \text{ The induced charge is given by } q = NBA/R = 50 \times 0.2 \times (100 \times 10^{-4}) / 2 = 0.5\text{c}$$

98. If $V_L = V_C$ then it is a case of resonance. Then V_L and V_C are out of phase Hence voltage across the resistance = source voltage = 100V

99. resistivity of a material depends on the temperature and independent of other physical conditions.

100. When a resistance wire cut in two pieces new resistance will be half the initial resistance. when these two are joined in parallel, $R_p = R/4$
 $Q_2/Q_1 = R_1/R_2 = R/(R/4) = 4$ therefore heat produced increases 4 times
