

# ELECTRO MAGNETIC INDUCTION


# Electro magnetic induction

**Faraday**




**1791 -1867**

**Henry**

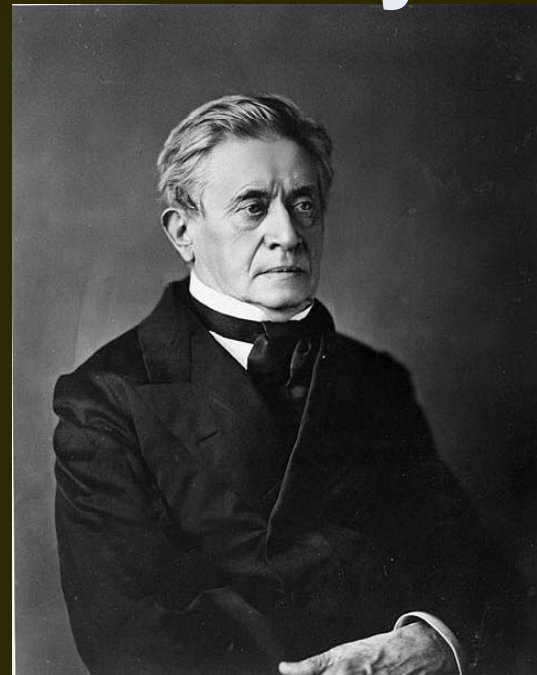


**1797 –1878**

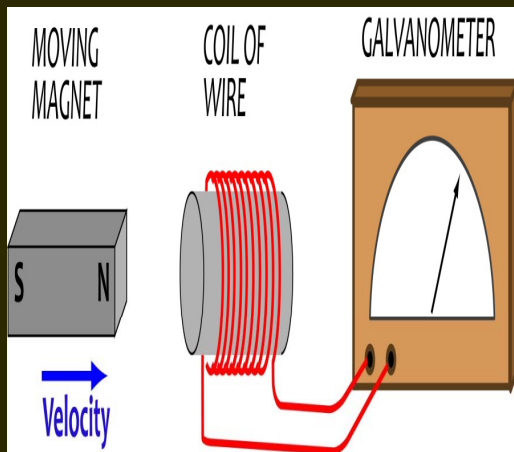

## Laws:-


### Faraday's Laws :-

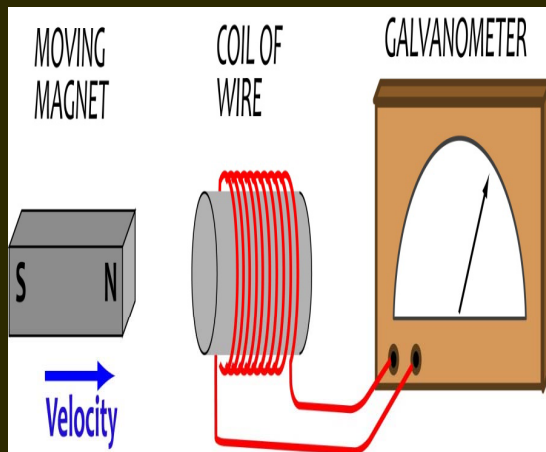
- 1) When ever there is a change in magnetic flux linked with a coil, a current is generated in the coil.



The current is called induced current and the emf responsible for the current is called induced emf. The phenomenon is called electro magnetic induction.

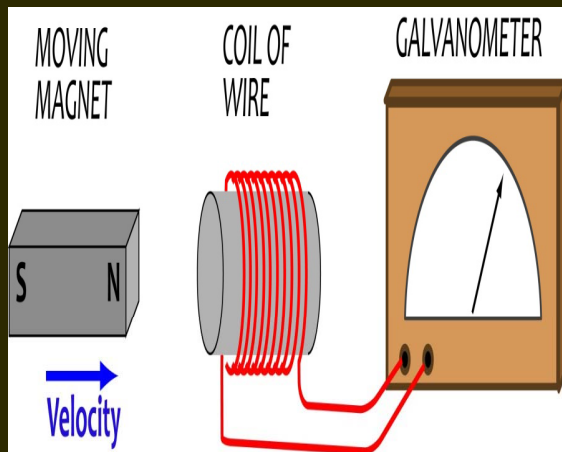**2) The induced emf (the induced current) is directly proportional to the rate of change of magnetic flux. (The emphasis is on the change of flux)**



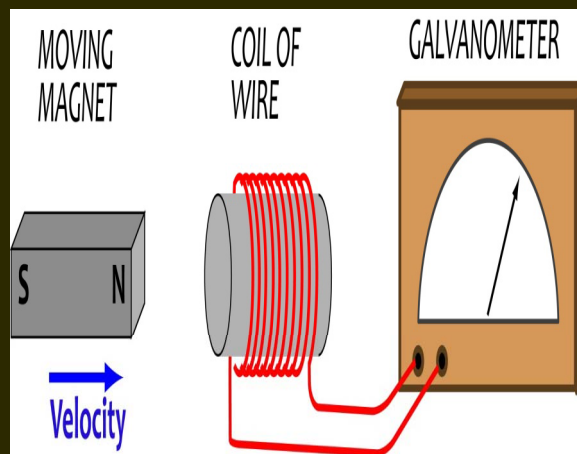


## Lenz's Law:-

The direction of the induced current (induced emf) is always to oppose the cause for which it is due. (Emphasis is on cause)

# Consequences of Electro magnetic induction.
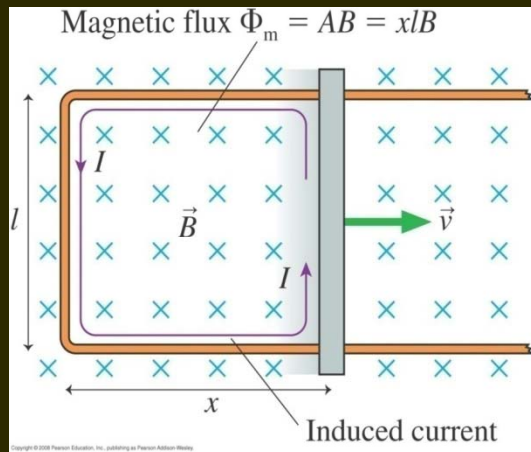
## Motional emf, Self induction, mutual induction and Eddy currents.



Motional emf =  $BLv$  volt.  
self inductance of a coil  
is  $L = \mu_0 \mu_r N^2 A$   
( $\mu_r$  is the relative permeability of the core),  
 $\mu_r = 1$  for air core

**Mutual- induction:** Between Pair  
of coils,  $M = \mu_0 \mu_r N_1 N_2 A$  henry  
( $\mu_r$  is the relative permeability of  
the core  $\mu_r = 1$ , for air core.)




## **Eddy currents :-**


**They are cyclic currents also called Foucault current in the bulk of a metal in a direction perpendicular to the magnetic flux. They cause heating effect and dissipate energy. This can be minimized by using laminated plates.**
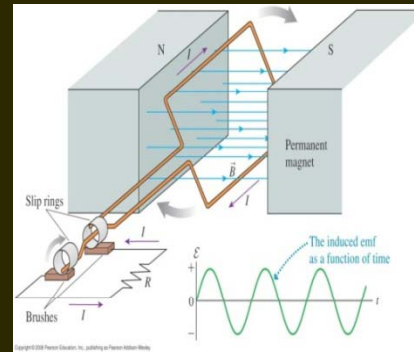
# Alternating current (Alternating voltage)

The current which oscillates between a positive maximum value and a negative minimum value is called alternating current(ac).The emf responsible is called alternating voltage.



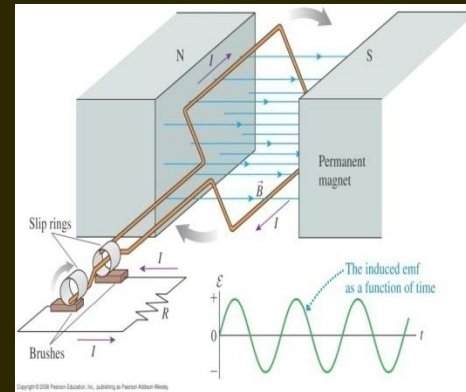$V = V_0 \sin \omega t$  is the  
expression for  
alt - voltage  
 $I = I_0 \sin \omega t$  is the  
expression for  
alt - current<sub>0</sub>



$e_0$  and  $i_0$  are the peak (max) values of the induced voltage and induced current respectively.

$\omega t = \sin^{-1} V / V_0$  or  $\omega t = \sin^{-1} I / I_0$  is called the phase. If  $\omega t$  is the same for current and voltage, then they are said to be in phase.

$$V_{ave} = (2/\pi)V_0, \quad I_{ave} = (2/\pi)I_0$$

$$V_{rms} = V_0 / \sqrt{2} \quad I_{rms} = I_0 / \sqrt{2}$$


$$P_{rms} = V_{rms} I_{rms}$$

$$P_{rms} = (V_0 / \sqrt{2}) \times (I_0 / \sqrt{2}) = V_0 I_0 / 2$$

**is called half power point in ac circuits**

# **AC applied to resistance, ideal inductance and ideal capacitance.**

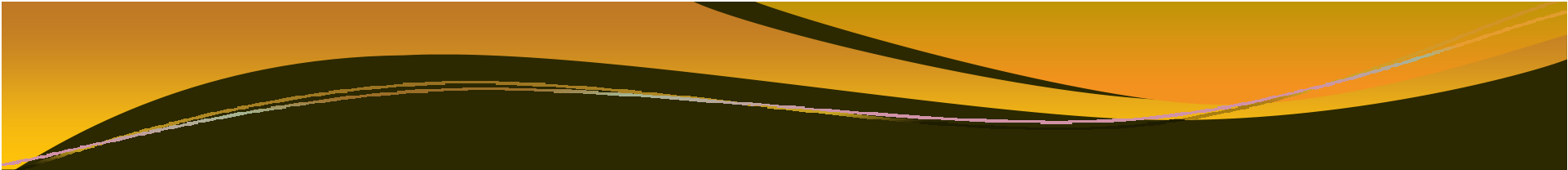**Ideal means inherent resistance of the circuit component is not considered for discussion. Power in AC circuits:-  $P_{ac} = V I \cos\phi$ .  $V = P D$  measured.  $I =$  Current measured ,  $\phi$  is the phase difference between voltage and current .**



**$\cos\phi$  is called the power factor in AC circuits because the magnitude of power transfer in AC circuits is dictated by  $\cos\phi$  .**

## AC applied to resistance

The behavior of resistance is identical for both AC and DC (we know that  $P_{dc} = \text{Voltage} \times \text{current}$ )



**The value of resistance is independent of frequency.**

**The voltage and current are always in phase in a resistance.**

**That means, in a purely resistive AC circuit ,ie.,  $\phi = 0$ ,**

**$\cos \phi = 1$  .  $P_{ac} = V I$  watt. In other**

**words For a resistance  $P_{dc} = P_{ac}$**

**The behavior of inductance for DC is transient where as for AC it is perpetual. It offers Inductive reactance  $X_L = \omega L = 2\pi fL$  ohm to AC.  $X_L \propto f$ , the frequency of the Applied AC.**

**The applied voltage and the  
resulting current through  
the pure inductance are not**

**In phase  $V = V_0 \sin \omega t$ .**


$$I = I_0 \sin (\omega t - 90^\circ), \phi = 90^\circ$$

The current lags behind the voltage by  $90^\circ$ .

$$P_{ac} = V I \cos \phi = P_{ac} = V I \cos 90^\circ$$

$$P_{ac} = 0 \text{ watt}$$

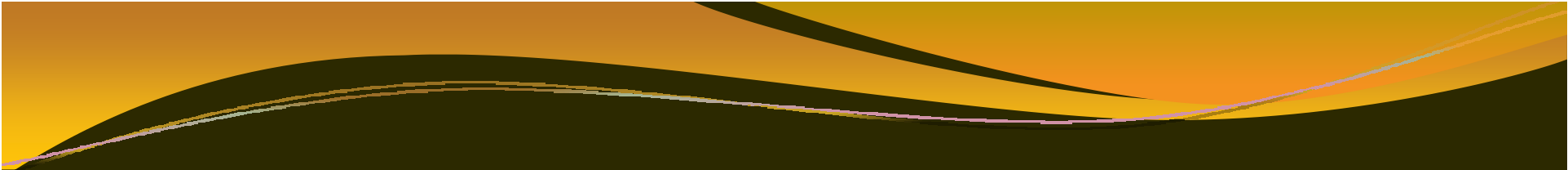The AC through an ideal inductance is called Watt less current.



**The behavior of capacitance to DC is instantaneous where it gets charged to the potential of applied DC voltage. When Alternating voltage is applied across 'C' its action becomes perpetual. It offers a capacitive reactance.**

$$X_c = 1/\omega C = (1/2\pi f C) \text{ ohm.}$$

$$\text{ie, } X_c \propto 1/f$$

$$V = V_0 \sin \omega t$$

$$I = I_0 \sin (\omega t + 90)$$

The applied voltage and the resulting current are not in phase.

The current leads the voltage by  $90^\circ$ .

## **Series RLC circuit**

**Here a resistance, an ideal inductance and an ideal capacitance are connected in series with a plug key. When the key is closed the source drives a current through the series combination and maintains an effective voltage  $V$  across the combination.**

The effective voltage can be obtained by a vector (phasor) diagram.  $V = \sqrt{V_R^2 + (V_L - V_C)^2}$   
 $V = I \sqrt{R^2 + (X_L - X_C)^2}$ ,  
 $V / I = Z$  ohm called the Impedance ( Effective resistance offered to AC by the series RLC circuit).  $Z = \sqrt{R^2 + (X_L - X_C)^2}$  ohm



## **Series resonant circuit**

**A series RLC circuit connected to an AC source of adjustable frequency (function generator) is called a series resonant circuit.**

**When the circuit is switched on, it drives a current through the circuit.**

**The magnitude of the current depends on the impedance  $Z$ .**

**But impedance depends on the values of  $R$ ,  $X_L$  and  $X_C$ .**

**$R$  is independent of frequency,**

**$X_L \propto f$  and  $X_C \propto 1/f$ .**

**$Z = \sqrt{\{R^2 + (X_L - X_C)^2\}}$  ohm.**


**At low frequencies of the applied**

**AC ( $X_C \gg X_L$ ),  $\sqrt{(X_L - X_C)^2}$  is very large , 'Z' is large and 'I' is small**

**At high frequencies of the applied**

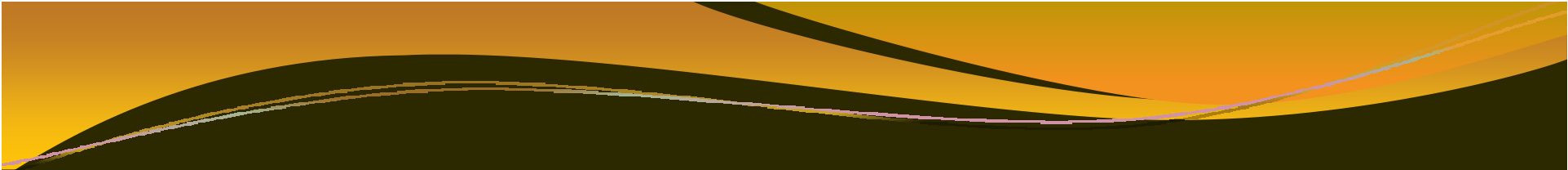**AC ( $X_L \gg X_C$ ),  $\sqrt{(X_L - X_C)^2}$  is again very large, Z is large 'I' is small .**

Therefore When frequency increases from a low value to a high value  $X_C$  decreases,  $X_L$  increases. At one particular frequency  $f_r$ ,  $X_L = X_C$ ,  $Z = Z_{\min} = R$ .  $I$  increases gradually And becomes maximum  $I = I_{\max}$  at  $f_r$ .



**This point of  $I = I_{\max}$  is called  
electrical Resonance and that  
particular frequency is called  
resonant frequency  $f_r$  .**

## Resonant frequency.

At  $f_r$ ,  $X_L = X_C$ ,  $Z = R$ , Power factor  
 $\cos\phi = R / Z$

$$2\pi f_r L = 1/2\pi f_r C \quad f_r = 1/2\pi\sqrt{LC}$$

### Q factor :-

$Q = (\text{Voltage across } L) / (\text{Voltage across } R)$   
at resonance.

$$Q = (V_L / V_R) = IX_L / IR = X_L / R$$

$$Q = 2\pi f_r L / R \quad \text{But } 2\pi f_r = 1 / \sqrt{LC}$$

$$Q = (L/R) \times (1 / \sqrt{LC}) = [\sqrt{L/C}] \times 1/R$$

**At half power frequency**


**$I = (I_{\max} / \sqrt{2})$ . Band width =  $f_2 - f_1$  and**

**$Q = f_r / (f_2 - f_1)$ . Q value is also called**

**the sharpness of resonance or**

**selectivity of the resonance circuit.**

**Q is large when R is small.**

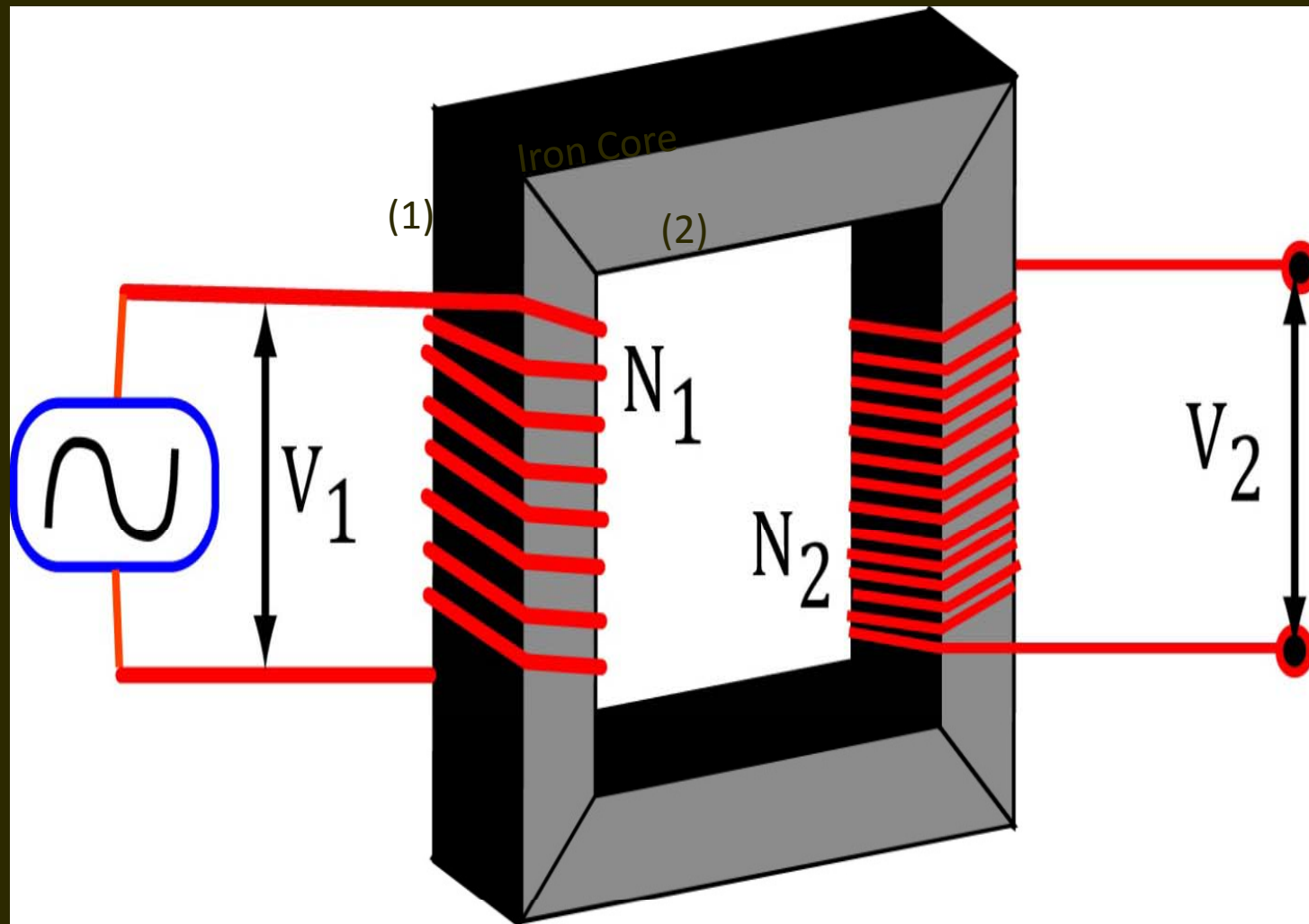



# Transformer

For an ideal transformer,

$$(V_2 / V_1) = (N_2 / N_1) = K$$

**K** is called Transformer turn ratio.

**$K > 1$   $N_2 > N_1$  it is called step up voltage transformer.**

**$K < 1$   $N_2 < N_1$  it is called step down voltage transformer.**

**$K = 1$   $N_2 = N_1$  it is called buffer transformer (Used in circuit isolation and impedance matching).**

**Input power = out put power**

$$V_2 I_2 = V_1 I_1$$